

Tube Distortion

by Ron Black Circuit from Guitar Player : October 1981

IC1 - 747 dual op-amp, others may be substituted but pinout will differ

IC2 - LM340K-12 Voltage Regulator

Bridge Rectifier - Full wave bridge recitifier, 50 Volts, 500 ma minimum

All resistors 1/2 W, 10% preferred

